

ANALOG AND DIGITAL SIGNAL PROCESSING

LABORATORY EXPERIMENTS : CHAPTER 3

Laboratory #1 – Chap 3

Linear System Response: general case

Objectives

- Understand the difference and the relationship between a step and impulse response.
- Determine the limits of validity of an approximated impulse response.

Theory

The idealized impulse function has some of the following properties :

$$\delta(t) = \lim_{a \rightarrow 0} \frac{u(t) - u(t - a)}{a} \quad \delta(t) = \frac{d}{dt} u(t)$$

R-C first order low-pass filter:

$$H(j\omega) = \frac{1}{1 + j\omega\tau} \implies H(s) = \frac{1}{1 + s\tau} = \frac{\frac{1}{\tau}}{s + \frac{1}{\tau}} \implies h(t) = \frac{1}{\tau} \cdot e^{-\frac{t}{\tau}} \cdot u(t)$$

<u>Function</u>	<u>Laplace Transform</u>	<u>Fourier Transform</u>
f(t)	F(s)	F(jω)
$d f(t)/dt$	$s F(s) - f(0^+)$	$j\omega F(j\omega)$
$\int_{-\infty}^t f(\tau) d\tau$	$F(s) / s$	$F(j\omega) / j\omega$
$\delta(t)$	1	1
1	1/s	-
e^{-at}	1/(s+a)	1/(jω+a)

Step Response: $Y(s) = H(s) / s \implies y(t) = \int h(\tau) d\tau$

Impulse Response: $h(t) = d y(t) / dt$


\implies *The linear system impulse response is the derivative of its step response*

ANALOG AND DIGITAL SIGNAL PROCESSING

LABORATORY EXPERIMENTS : CHAPTER 3

Procedure

1) Build the following R-C circuit:

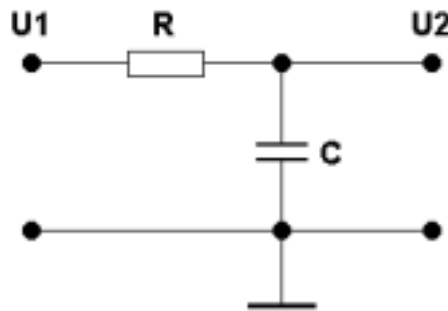

With: $R = \quad \Omega$, $C = \quad \text{nF} \implies \tau = R \cdot C = \quad \text{s}$

2) $u_1(t)$ is a square-wave with $u_{1\text{low}} = 0\text{V}$ and $u_{1\text{high}} = 1\text{V}$, 50% duty cycle.

Choose an appropriate frequency in order to make sure that the period is at least equal to $10 \cdot \tau$. Verify that $u_2(t)$ is equal to the integral of this circuit impulse response! i.e:

$$u_2(t) = 1 - e^{-t/\tau} \quad (\text{rising edge at } t = 0)$$

$$u_2(t) = e^{-(t-t_0)/\tau} \quad (\text{falling edge at } t = t_0)$$

3) What happens if the square-wave frequency is not chosen correctly?

4) $u_1(t)$ is a rectangle pulse with $u_{1\text{low}} = 0\text{V}$ and $u_{1\text{high}} = 1\text{V}$.

$$\text{ON-time: } t_{\text{on}} = \tau / 10 \quad \text{OFF-time: } t_{\text{off}} = 10 \cdot \tau$$

Verify that $u_2(t)$ is approximately equal to the impulse response of this circuit

Remember the scaling factor!!!

5) What happens if t_{on} and t_{off} are not chosen correctly?

Consider several situations.

ANALOG AND DIGITAL SIGNAL PROCESSING

LABORATORY EXPERIMENTS : CHAPTER 3

Laboratory #2 – Chap 3

Linear System Response: general case

Objectives

- Apply the Laplace Transform theory in a practical example.
- Understand the relationship between a filter bandwidth and its rise and/or fall time (transient mode)

Theory

From Laplace Transform theory: $u_2(t) = L^{-1} [L[u_1(t)] \cdot L[h(t)]] = L^{-1} [U_1(s) \cdot H(s)]$


$h(t)$: second order band-pass filter ($R_p \rightarrow \infty$), $u_1(t)$: unit step: $\Rightarrow U_1(s) = 1/s$

$$H(s) = \frac{\frac{S \cdot L \cdot \frac{1}{S \cdot C}}{S \cdot L + \frac{1}{S \cdot C}}}{R_1 + \frac{S \cdot L \cdot \frac{1}{S \cdot C}}{S \cdot L + \frac{1}{S \cdot C}}} = \frac{\frac{1}{C \cdot R} \cdot s}{s^2 + \frac{s}{C \cdot R_1} + \frac{1}{L \cdot C}} \quad \Rightarrow \quad Y(s) = \frac{1}{s} \cdot H(s) = \frac{\frac{1}{C \cdot R} \cdot s}{s^2 + \frac{s}{C \cdot R_1} + \frac{1}{L \cdot C}}$$

From Laplace Transform table: $k \cdot \frac{\omega_0}{(s^2 + a)^2 + \omega_0^2} \Rightarrow k \cdot e^{-a \cdot t} \cdot \sin(\omega_0 \cdot t) = k \cdot e^{-\frac{t}{\tau}} \cdot \sin(\omega_0 \cdot t)$

After some algebra: $k = \frac{1}{\sqrt{\frac{C \cdot R_1^2}{L} - \frac{1}{4}}}$ $a = \frac{1}{2 \cdot C \cdot R_1}$ $\tau = 2 \cdot C \cdot R_1$ $\omega_0 = \sqrt{\frac{1}{L \cdot C} - \frac{1}{4 \cdot C^2 \cdot R_1^2}}$

Example:

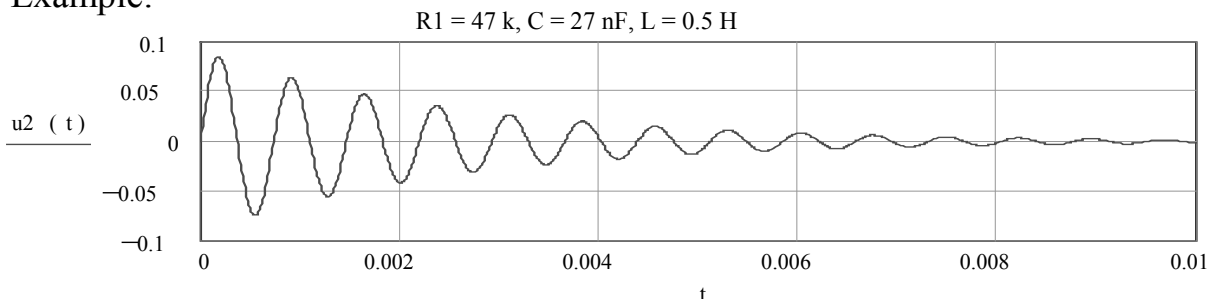


$k = 0.092 \quad \tau = 2.53 \text{ ms} \quad f_0 = 1.37 \text{ kHz}$

ANALOG AND DIGITAL SIGNAL PROCESSING

LABORATORY EXPERIMENTS : CHAPTER 3

Procedure

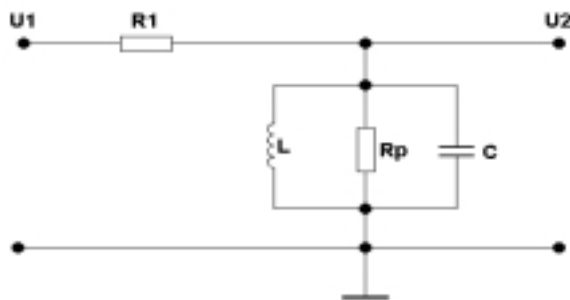- 1) Build the following second order R-L-C band-pass filter:



$$R1 = \quad k\Omega \quad L = \quad H \quad C = \quad nF$$

$$\Rightarrow f_0 = \quad kHz,$$

$$Bw \approx 1/(2 \cdot \pi \cdot Req \cdot C) = \quad Hz$$

(with $Q = f_0/Bw > 5$)

- 2) $u_1(t)$ is a square-wave with $u_{1\text{low}} = 0V$ and $u_{1\text{high}} = 1V$, 50% duty cycle. Choose an appropriate frequency in order to make sure that the period is at least equal to $5/Bw$. Measure k , τ and f_0 and compare your results with the theoretical values.
- 3) What happens if the square-wave frequency is not chosen correctly?
- 4) With the same signal generator parameters, divide $R1$ by 3. What happens?
- 5) With the same signal generator parameters, divide $R1$ by 10. What happens?
- 6) Impulse response measurement: From theory, we know that:

$$h(t) = \frac{d}{dt} y_{\text{step}}(t) = k \cdot e^{-\frac{t}{\tau}} \cdot \left(\omega_0 \cdot \cos(\omega_0 \cdot t) - \frac{1}{\tau} \cdot \sin(\omega_0 \cdot t) \right)$$

$$\text{if } \omega_0 > 10 \cdot \frac{1}{\tau} \Rightarrow h_{\text{approx}}(t) = k \cdot \omega_0 \cdot e^{-\frac{t}{\tau}} \cdot \cos(\omega_0 \cdot t)$$

$u_1(t)$ is a rectangle pulse with $u_{1\text{low}} = 0V$ and $u_{1\text{high}} = 1V$.

ON-time: $t_{\text{on}} = 1 / (20 \cdot f_0)$ OFF-time: $t_{\text{off}} = 5 \cdot Bw$

Verify that $u_2(t)$ is approximately equal to the impulse response of this circuit

Remember the scaling factor !!!

- 7) What happens if t_{on} and t_{off} are not chosen correctly?
Consider several situations.
- 8) Apply a FSK signal (VCF input of your function generator driven by a square-wave of appropriate amplitude and frequency!) to your band-pass filter. Determine the fastest data rate allowing data recovery. Conclusion?

Choose: $\text{freq}_{\text{high}} \approx 1.5 \text{freq}_{\text{low}}$, $\text{freq}_{\text{high}} = f_0$

ANALOG AND DIGITAL SIGNAL PROCESSING

LABORATORY EXPERIMENTS : CHAPTER 3

Laboratory #3 – Chap 3

Linear System Response: general case

Objectives

- Understand multiplication in the time domain and the corresponding convolution in the frequency domain.
- Verify that the product of two periodic signals generates sums and differences of frequencies contained in the periodic signals.

Theory


$$y(t) = x_1(t) \cdot x_2(t)$$

$$x_1(t) = A_1 \cdot \sin(2 \cdot \pi \cdot \text{freq}_1 \cdot t), \quad x_2(t): \text{symmetrical square-wave of frequency } \text{freq}_2$$

$$y(t) = A_1 \cdot \sin(2 \cdot \pi \cdot \text{freq}_1 \cdot t) \cdot A_2 \cdot \sum_{n=1}^{10} \frac{1}{2 \cdot n - 1} \cdot \sin[2 \cdot \pi \cdot \text{freq}_2 \cdot (2 \cdot n - 1) \cdot t]$$

$$A_1 = 1 \quad A_2 = 1$$
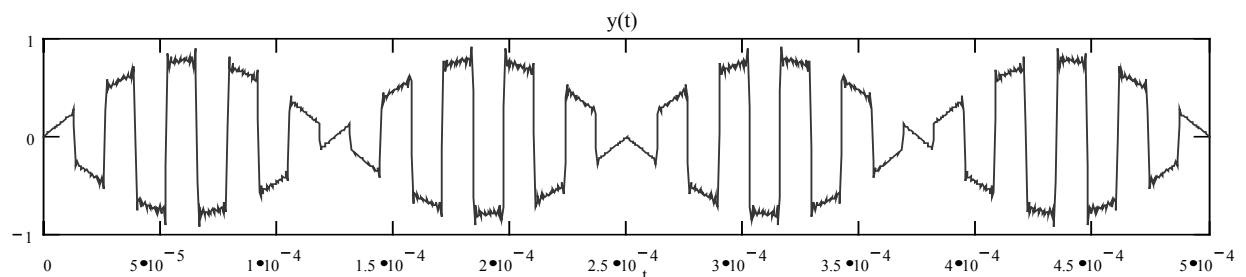
$$\text{freq}_1 = 4 \cdot 10^3 \quad \text{freq}_2 = 3.8 \cdot 10^4$$




Time domain analysis:

$$\text{Reminder: } \sin(a) \sin(b) = 0.5 [-\cos(a+b) + \cos(a-b)]$$

Frequency components of $y(t)$:

1.38 kHz \pm 4 kHz	relative amplitude: 1
3.38 kHz \pm 4 kHz	1/3
5.38 kHz \pm 4 kHz	1/5
m.38 kHz \pm 4 kHz	1/m

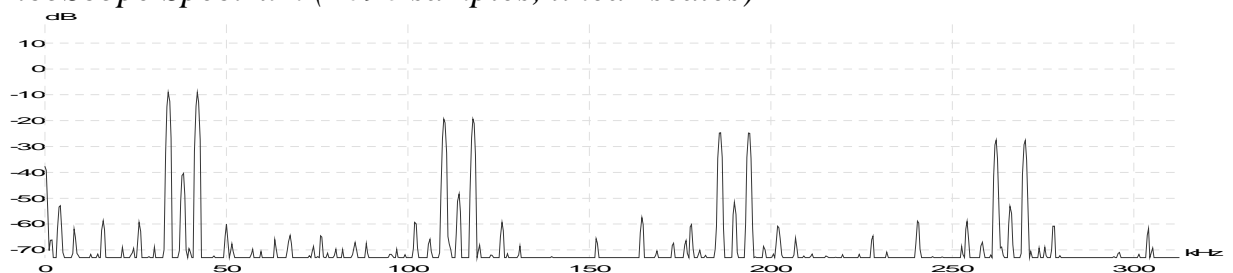PicoScope Spectrum (4096 samples, linear scales)




ANALOG AND DIGITAL SIGNAL PROCESSING

LABORATORY EXPERIMENTS : CHAPTER 3

Frequency domain analysis (convolution):


Concept:

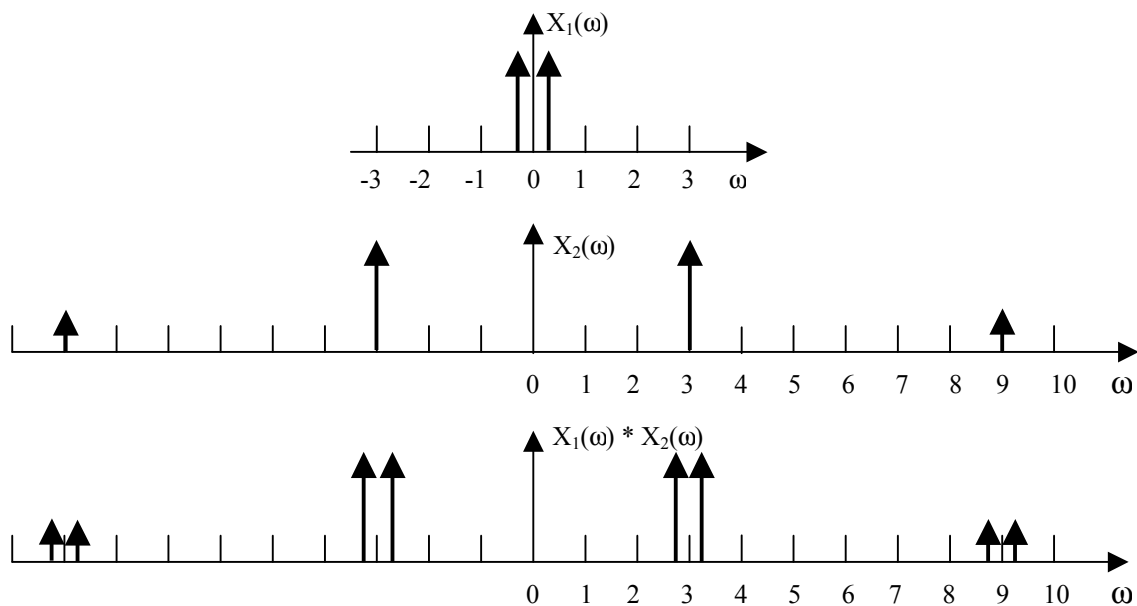


Procedure (with AMPMIX board)

Board extra-gain: 0 dB, Band-pass filter: OFF

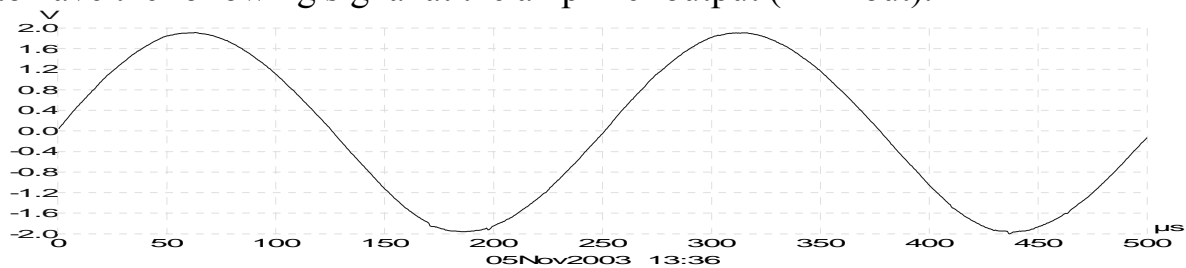Input a 4 kHz sine-wave to the AMPMIX board (Input). Adjust its amplitude so as to have the following signal at the amplifier output (AMPout):



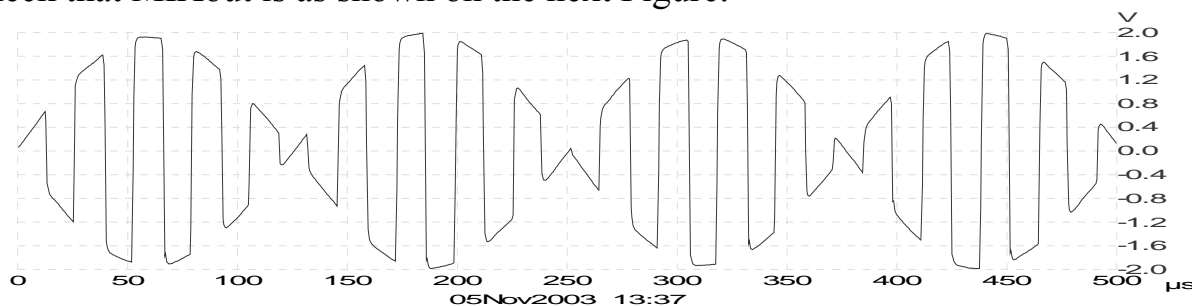Check that MIXout is as shown on the next Figure:



Use “PicoScope Spectrum Analyser” (No of spectrum bands: 4096, 1.5 MHz) to compare your display with the theory.

ANALOG AND DIGITAL SIGNAL PROCESSING

LABORATORY EXPERIMENTS : CHAPTER 3

Laboratory #4 – Chap 3


Linear System Response: general case

Objectives

- Understand “*Frequency down-conversion*”.
- Verify that “*undesired frequencies (e.g. mirror image)*” can also convert down to *base-band*.

Theory

“AMP MIX” board bloc diagram:

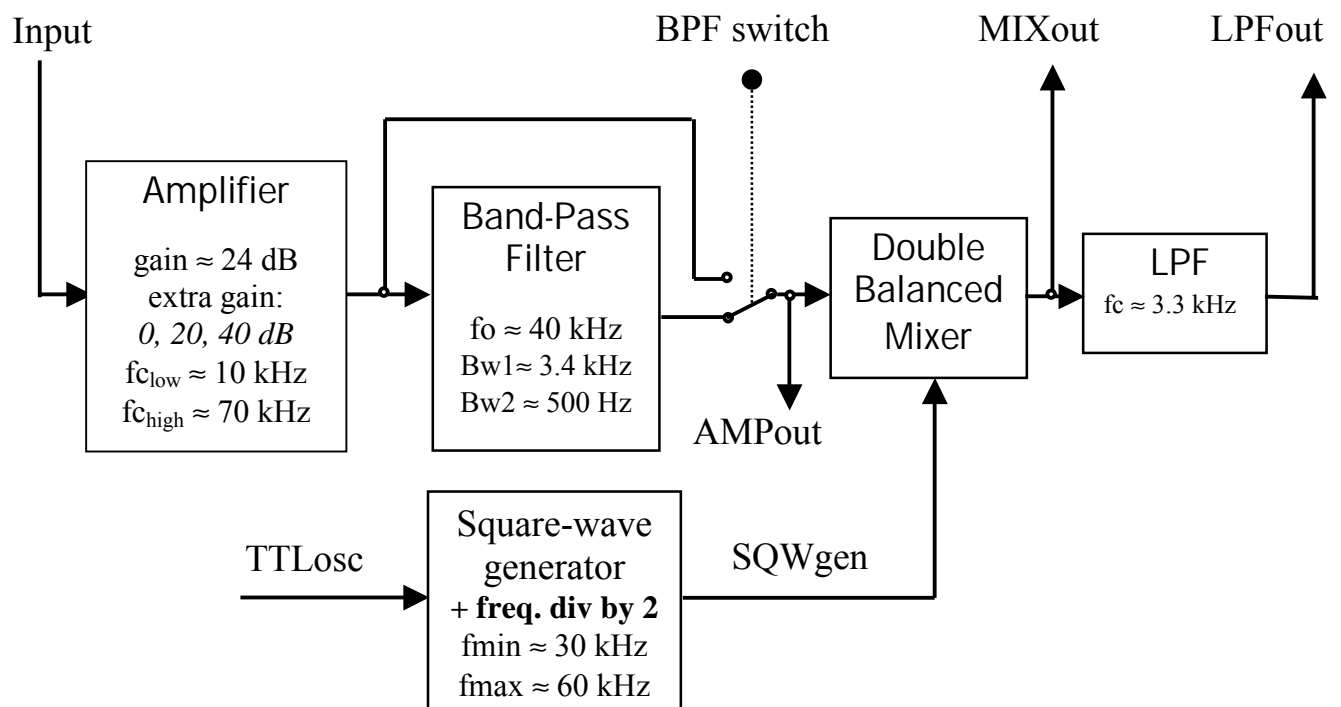

Power supply: 5 (8 mA) to 18V (20 mA), Input impedance: 5 k Ω (AC coupling)

Amplifier: $f_{c_{low}} \approx 10$ kHz, $f_{c_{high}} \approx 70$ kHz
gain: ≈ 24 dB, additional gain: + 20 dB or + 40 dB

Band-Pass filter: Second order, resonant frequency adjustable around 40 kHz.
Bandwidth: *Wide* (3.4 kHz) or *Narrow* (≈ 500 Hz)

Square-Wave generator: Tunable $f_{min} \approx 30$ kHz, $f_{max} \approx 60$ kHz
External frequency control (TTLOsc), $SQW_{gen_{freq.}} = TTLOsc_{freq.}/2$

Double balanced mixer: $MIXout(t) = AMPout(t) \cdot SQWgen(t)$, i.e. AMPout multiplied by ± 1

LPF: Three cascaded R-C low-pass filters

ANALOG AND DIGITAL SIGNAL PROCESSING

LABORATORY EXPERIMENTS : CHAPTER 3

Procedure (with AMPMIX board)


Part 1:

Input: sine-wave - 40 kHz - 100 mV peak-to-peak

Extra gain: *OFF* BPF: *OFF* SQWgen: *Local* (≈ 38 kHz)

Verify:

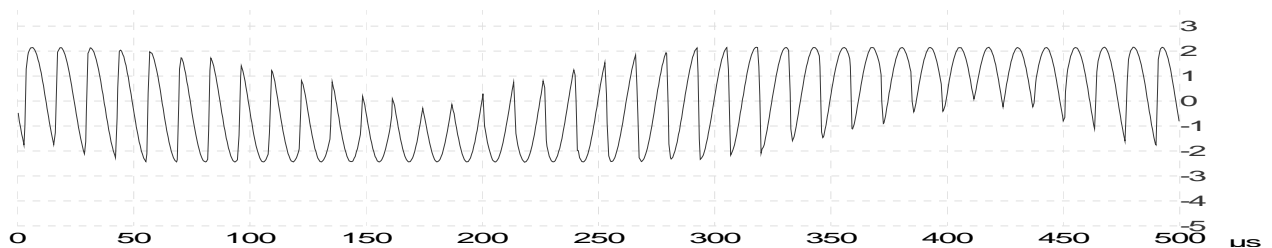- AMPout: "clean" 40 kHz sine-wave (i.e. no saturation), ≈ 1.6 V pp
- MIXout: must look as follows:



- LPFout: "clean" 2 kHz sine-wave, amplitude: ?
- Change the input sine-wave frequency in order to determine the output LPF cut-off frequency.
- Verify the "mirror" frequency concept (i.e. input signal frequency ≈ 36 kHz).
- Verify that if the input signal frequency is 2 kHz higher (or lower) than a local oscillator harmonic", then down-conversion does occur and LPFout is also a 2 kHz sine-wave. What can you say of LPFout signal amplitude?


Part 2:

Input: FSK (freq_L: 30 kHz and freq_H: 40 kHz), 1000 bits/s - 100 mV pp

Extra gain: *OFF* BPF: *OFF* SQWgen: *Local* (≈ 38 kHz)

Verify:

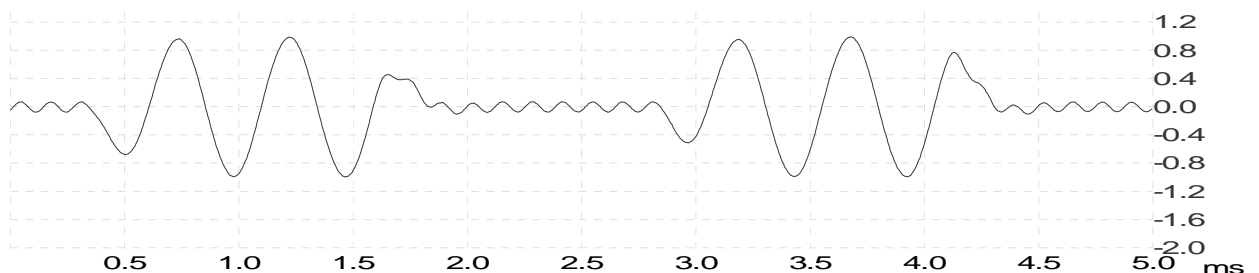- AMPout: "clean" 30 kHz and 40 kHz sine-wave (i.e. no saturation)
- LPFout looks as follows:



- Explain why!
- Slowly decrease freq_H. What happens?

ANALOG AND DIGITAL SIGNAL PROCESSING

LABORATORY EXPERIMENTS : CHAPTER 3

Laboratory #5 – Chap 3

Linear System Response: general case

Objectives

- Understand..... Band-Pass Filter rise-time
- Prove.....

Theory

.....

Procedure

.....

.....